
EE537 Circuit Simulation Lab

Experiment 9

Name: <GANGADHAR GUPTA>

ID Number: <2023eem1037>

November 14, 2023

1 Layout of an inverter

Create a Layout of an inverter with the PMOS transistor of (4u/1u) and NMOS transistor of (2u/1u). Present the pre-layout and post-layout simulation result of your inverter.

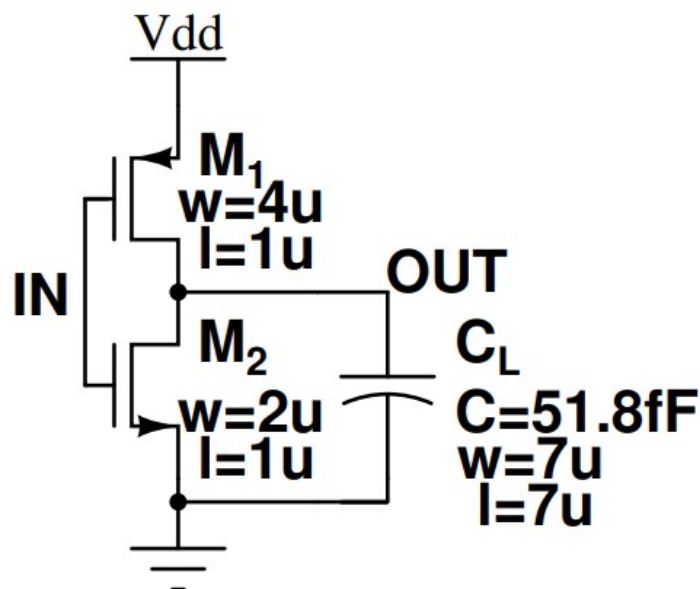


Figure 1: Schematic of an inverter

- schematic

 


Figure 2: schematic of inveter

- testbench

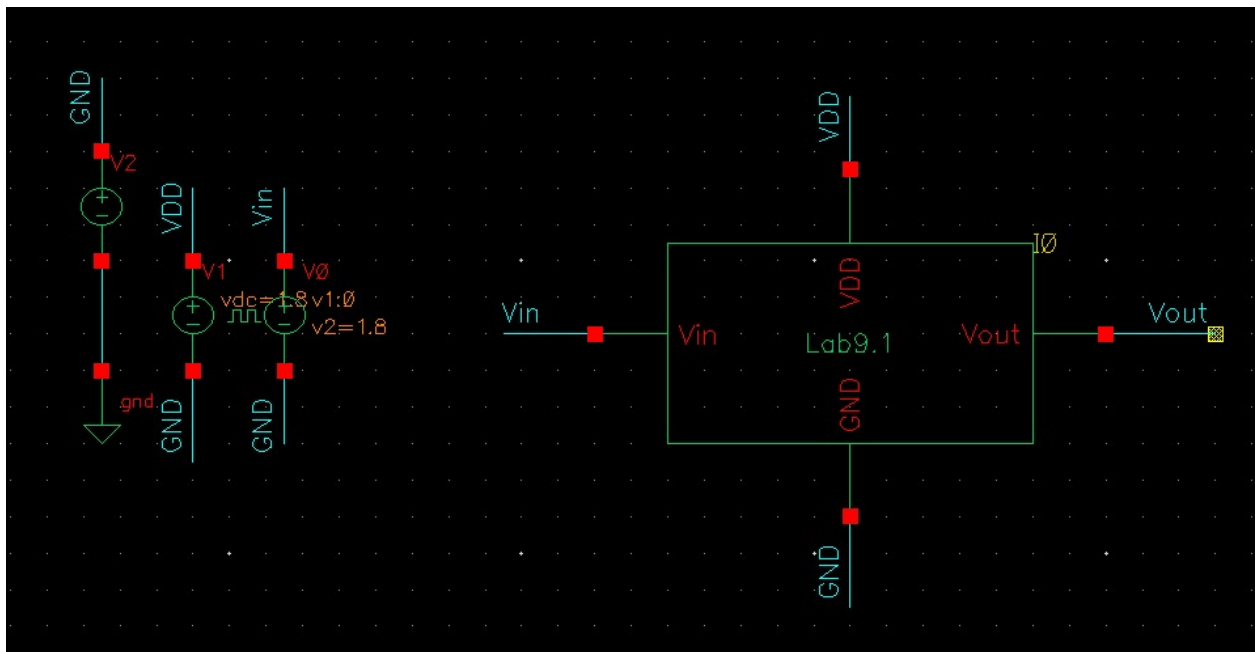


Figure 3: testbench of the inverter

- Layout

 


Figure 4: layout of the inverter

- AV extracted layout

 


Figure 5: AV extracted layout of the inverter

- design run check

 


Figure 6: drc of the inverter

- layout vs schematic

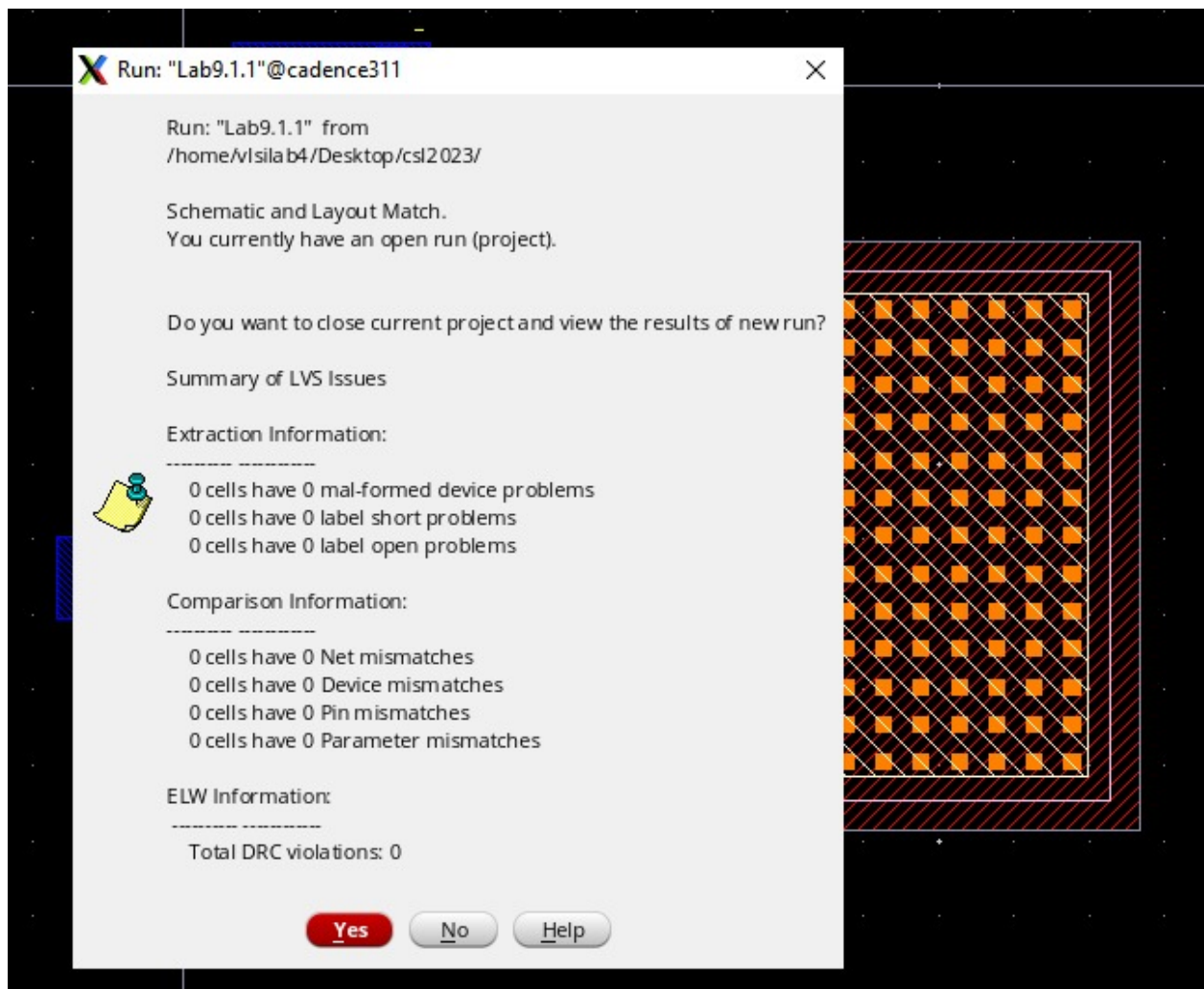


Figure 7: lvs of the inverter

- pre and post layout

 


Figure 8: output of the pre layout and post layout

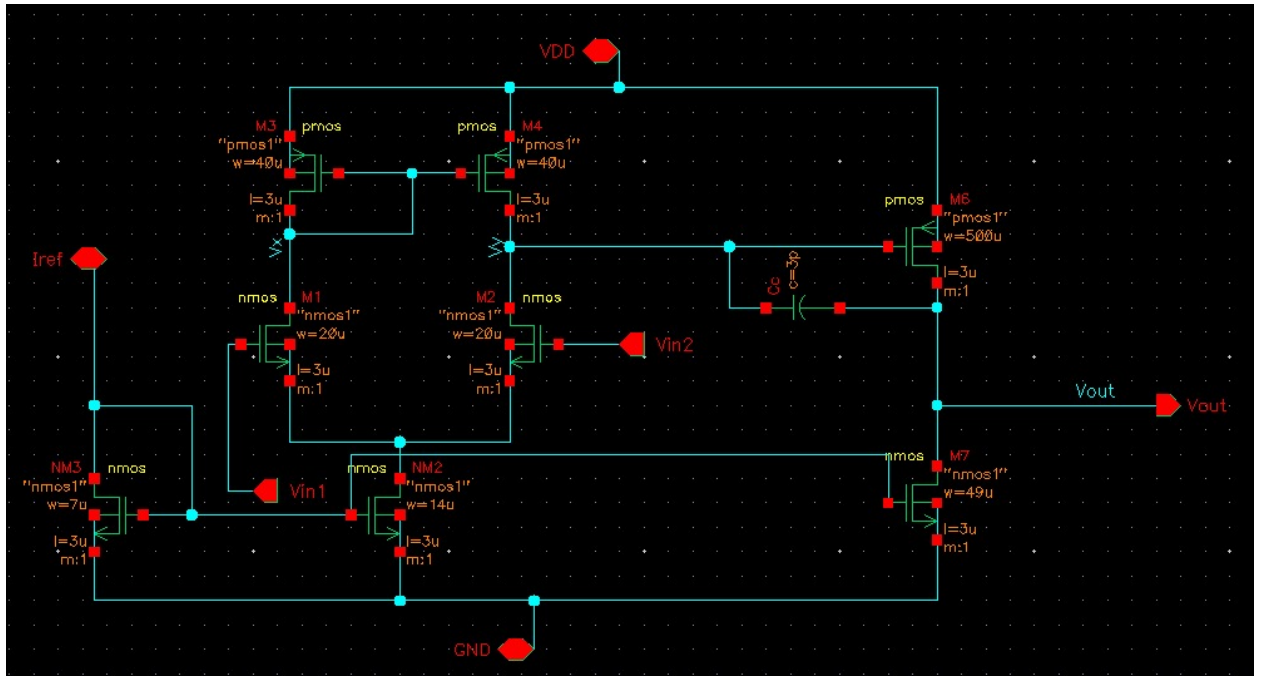


Figure 9: Ota schematic

 


Figure 10: ota layout